- -

3.2.2

: 01-909

2020

: , .


: , , , , , , , .

1

 $\cdot \qquad , \quad \ \ \, - \quad , \qquad - \quad , \qquad \cdot \qquad , \quad \cdot \qquad .$

Ζ,
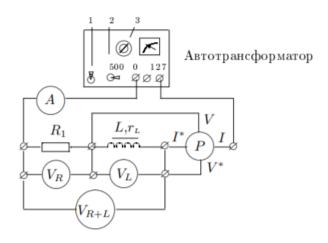
$$Z = R + i(\omega L - \frac{1}{\omega C}) \tag{1}$$



. 1:

$$U_R = IR \tag{2}$$

$$U_L = I\sqrt{r_L^2 + (\Omega L)^2} \tag{3}$$

$$U_{L+R} = I\sqrt{(r_L + R)^2 + (\Omega L)^2}$$
 (4)

, , .

$$P_L = U_L \cdot I \cdot \cos(\psi) = I^2 \cdot r_L \tag{5}$$

, , , .
$$r_L, , - \qquad \qquad \mathbf{R} \quad (.2). , \qquad \Omega \quad (\qquad \omega_0 = \Omega), \qquad :$$

$$\omega_0 \cdot L = \frac{1}{\omega_0 \cdot C} \tag{6}$$

- Q , R_{sum} ,:

$$Q = \frac{\omega_0 L}{R_{sum}} = \frac{1}{\omega_0 C R_{sum}} \tag{7}$$

 R_{sum} R r_L

$$R_{sum} = R + r_L \tag{8}$$

. 2:

2

$$U_{\sum,res} = I_{res} \cdot R_{\sum} \tag{9}$$

$$U_{C,res} = \frac{I_{res}}{\Omega \cdot C} \tag{10}$$

(6), (7) (8), :

$$Q = \frac{U_{C,res}}{U_{\sum,res}} \tag{11}$$

. , R_{\sum} (6), r_L (8),

3

3.1

1) , , (2) (3) $r_L L$.

$$r_L = \frac{P_L}{I^2} \tag{12}$$

$$L = \frac{1}{\Omega} \cdot \sqrt{\left(\frac{U_L}{I}\right)^2 - r_L^2} \tag{13}$$

$$\sigma_{r_L} = r_L \cdot \sqrt{\left(\frac{\sigma_{P_L}}{P_L}\right)^2 + 4 \cdot \left(\frac{\sigma_I}{I}\right)^2} \tag{14}$$

$$\sigma_L = L \cdot \sqrt{\left(\frac{\sigma_{P_L}}{P_L}\right)^2 + 4 \cdot \left(\frac{\sigma_I}{I}\right)^2} \tag{15}$$

1.

$$r_L = 9.2 \, Om, \ L = 1.09 \, H$$

$$\sigma r_L = 0,27 \ Om, \ \sigma_L = 0.03 \ H.$$

L(x) $r_L(x)$

3.2

			1:			
x_{disp}	I,	U_R ,	U_L ,	U_{L+R} ,	P_L ,	L, H
0,5	0,825	73	77	115	11,25	2,40
0,7	0,875	78,5	68	113	10	2,10
0,9	0,925	82,5	63	112	9,5	1,87
1,1	0,95	85,5	58	111	9	1,69
1,3	0,975	88	54	110,5	8,75	1,58
1,5	1,0125	90	51	110	8,25	1,46
1,7	1,02	91	48,5	110	8	1,38
1,9	1,025	92	46	109	7,75	1,31
2,1	1,028	92,5	44	109	7,5	1,24

2	$2: r_L I$	L (3) (5)
	L, H	r_L , Om
	1,84	16,53
	1,53	13,06
	1,34	11,1
	1,2	9,97
	1,09	9,2
	0,99	8,05
	0,94	7,69
	0,89	7,38
	0,84	7,1

 ψ :

$$cos\psi = 0.88$$


:

$$U_{L,act} = U_{L+R} \cdot \cos\psi - U_R = 9,24V$$

$$U_{L,react} = U_{L+R} \cdot sin(\psi) = 52,47V$$

:
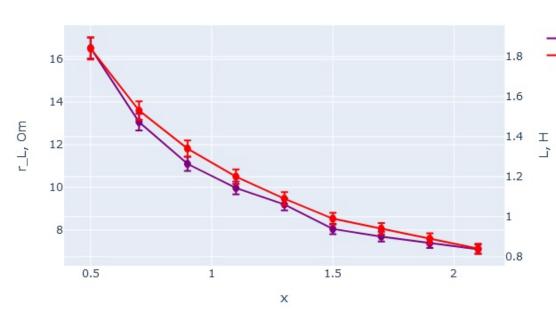
$$L = \frac{U_{L,react}}{I\Omega} = 1,02H$$



(1).jpg(1).bb

. 3:

$$r_L = \frac{U_{L,act}}{I} = 9,48Om$$

:

$$\sigma_{r_L} = r_L \cdot \sqrt{\left(\frac{\sigma_{U_{L,act}}}{U_{L,act}}\right)^2 + \left(\frac{\sigma_I}{I}\right)^2}$$
 (16)

.


$$\sigma_L = \sigma_{U_{L+R}} + \sigma_{U_R} \tag{17}$$

(16), (17), :

3.3

 P_L P_L :

$$P_L = I \cdot U_L \cdot cos(\theta)$$

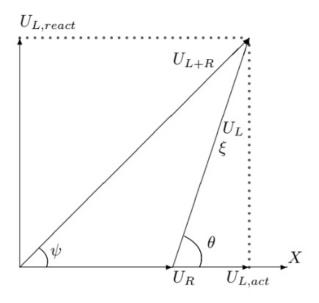

. 4:

$$I = \frac{U_R}{R_1} \approx 0.89 A$$
$$U_L \cdot cos(\theta) = U_{L,act}$$

, :

$$P_L = 0.89 \ A \cdot 9.24 \ V \approx 8.22 \ Watt$$

$$P_{L,Vect} \approx 8.22 \mbox{ Watt.}$$

$$P_L = 8.75 \mbox{ Watt.} \ , \qquad \mbox{5-} \ . \label{eq:PL}$$

3.4

 r_L

$$r_L = \frac{U_{\sum,res}}{I_{res}} - R_2 = 12.67 \, Om$$

	$3: r_L$	
I,	U_{\sum} ,	r_L , Om
3,35	62	12,67

3.5

$$L$$
 r_L Q (Q (8))
$$L = \frac{1}{\omega_0^2 \cdot C} \approx 12.8 H$$

$$r_L = \frac{\omega_0 L}{Q} - R = 12,8 Om$$

3.6

 $L r_L$

4 : L r_L							
	.(0 Hz)	LCR		$f(I, U_{\sum})$	f(Q)		
r_L , Om	2.09	9.2	9.48	12.67	12.8		
L, H	-	1.6	1.02	-	1.8		

4